



Analysis of Circuits Effects in Analog Devices

ROCHE Nicolas

nicolas.roche@ies.univ-montp2.fr

Équipe **RADIAC** « **RADI**ation et **Composants** »
Institut d'Électronique du Sud (IES)







Introduction

- **ICs in Bipolar** technology Exhibit degradation with TID
- Both **electrical** and **functional parameters** are impacted: I_{in} ↗ I_{cc} ↘
- In Physics oriented studies, the **input bias current** is often used to evaluate the degradation
- Problem: The degradation curves exhibit a **variety of shapes**
- What are the root **causes**?
- What are the **consequences** for **RHA**?

Starting point

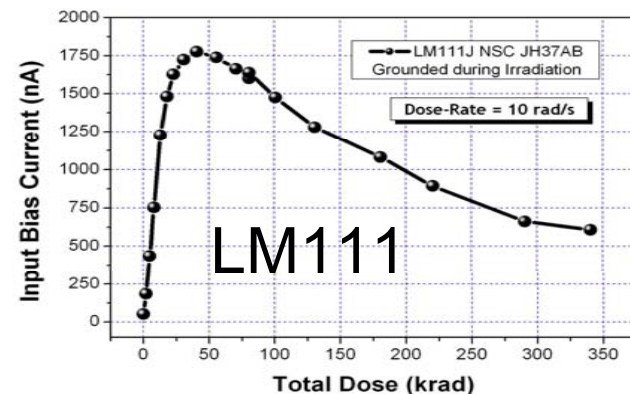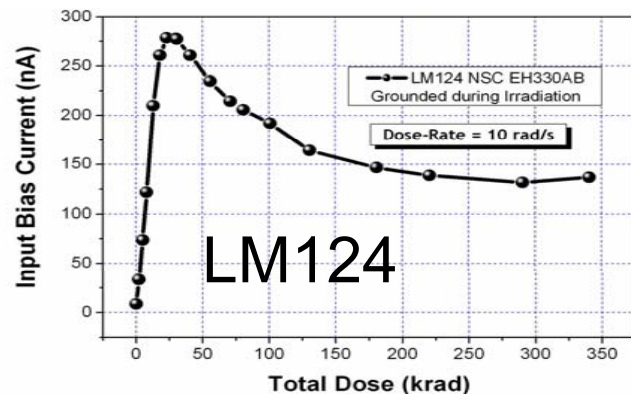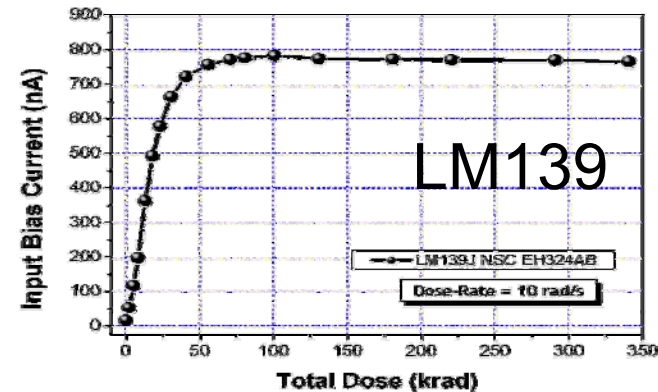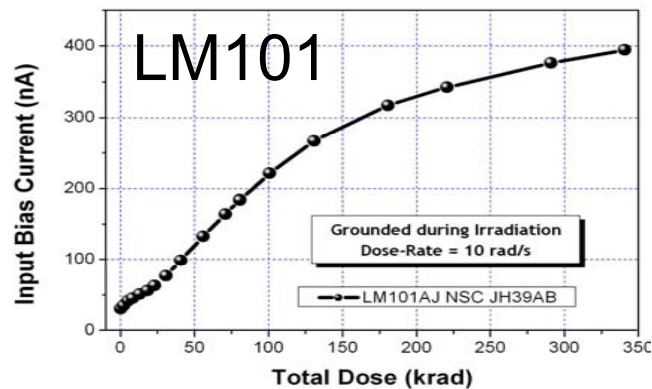4 ICs irradiated @ 11 rad/s → 4 different responses




Compensation mechanisms

- In a bipolar Junction Transistor:

- TID $\rightarrow I_b \nearrow$ & $\beta \searrow$


$$I_b = \frac{I_c}{\beta}$$

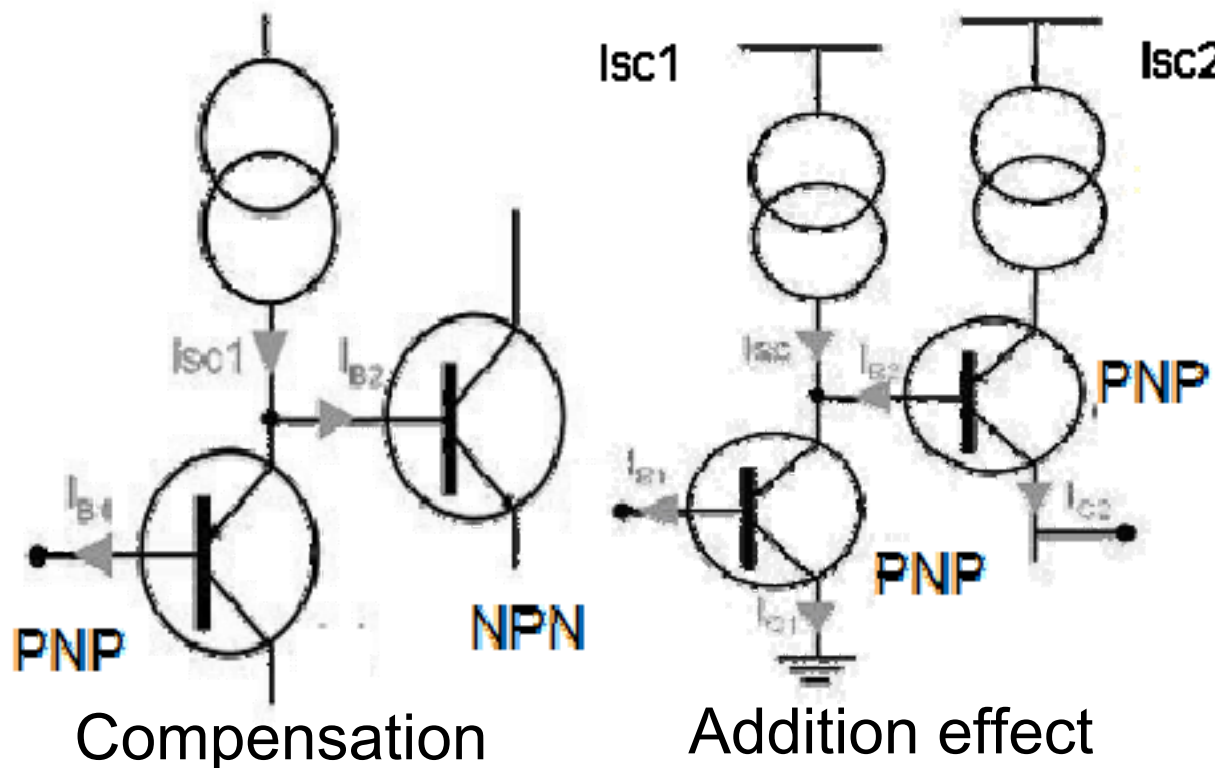- In a circuit, I_c is forced with a current source I_{sc}
- Connections at the collector node may derive or add current




$$I_{in} = \frac{I_{sc} \pm I_{b2}}{\beta}$$

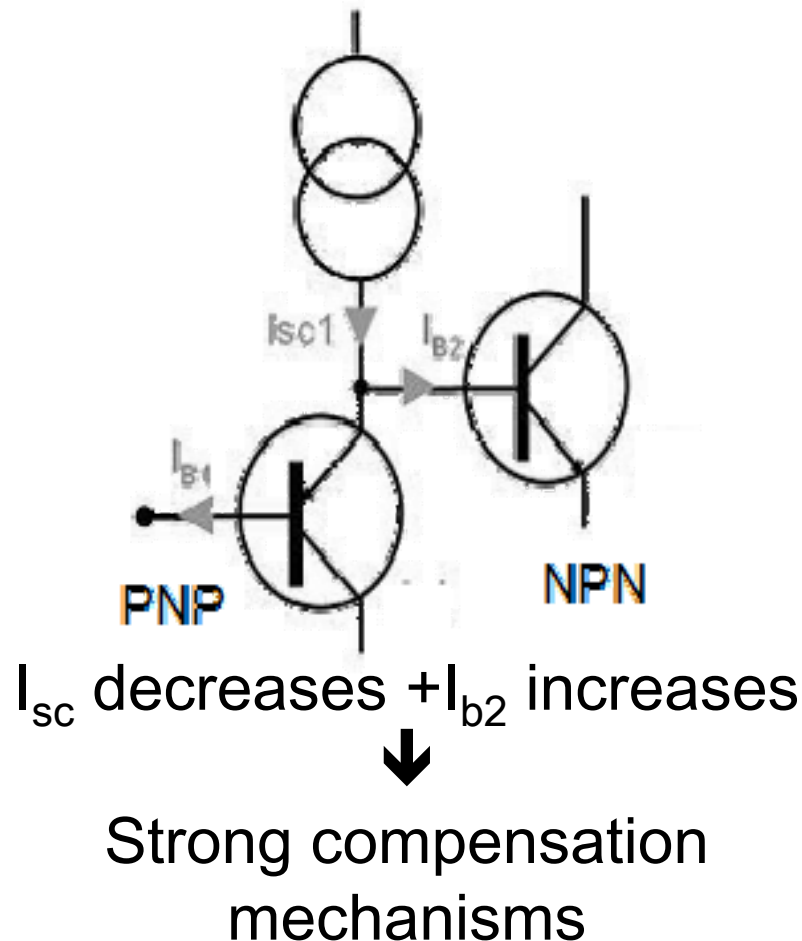Example of Circuit Effect and Compensation Mechanism in the LM111*


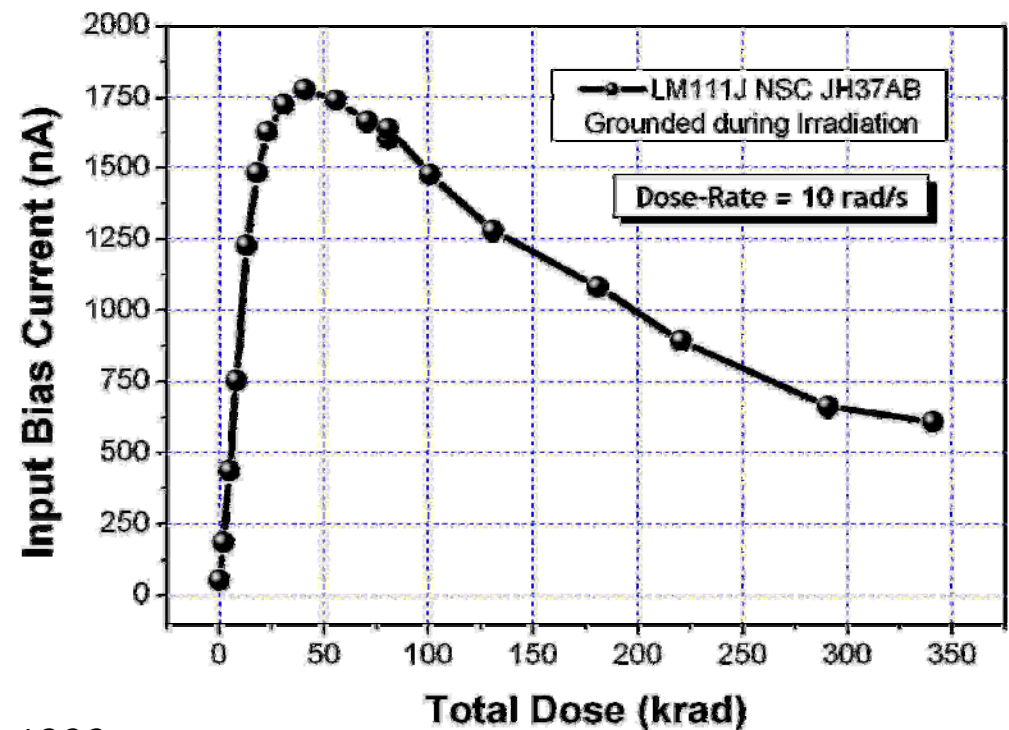
$$I_{in}(D) = \frac{I_{sc1}(D) - I_{b2}(D)}{\beta_1(D)}$$






* H. Barnaby et al. IEEE Trans. Nuc. Sci Dec 1999

Same structure

LM139


LM124

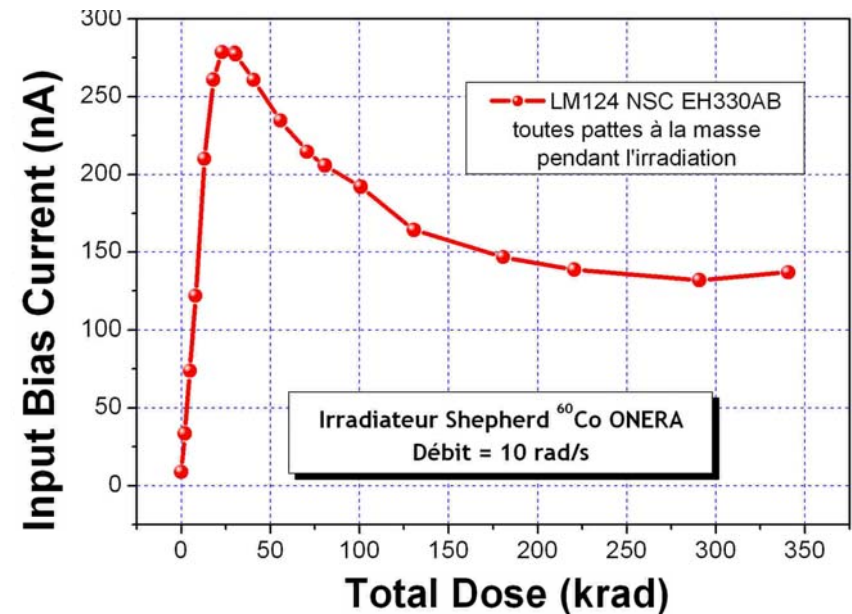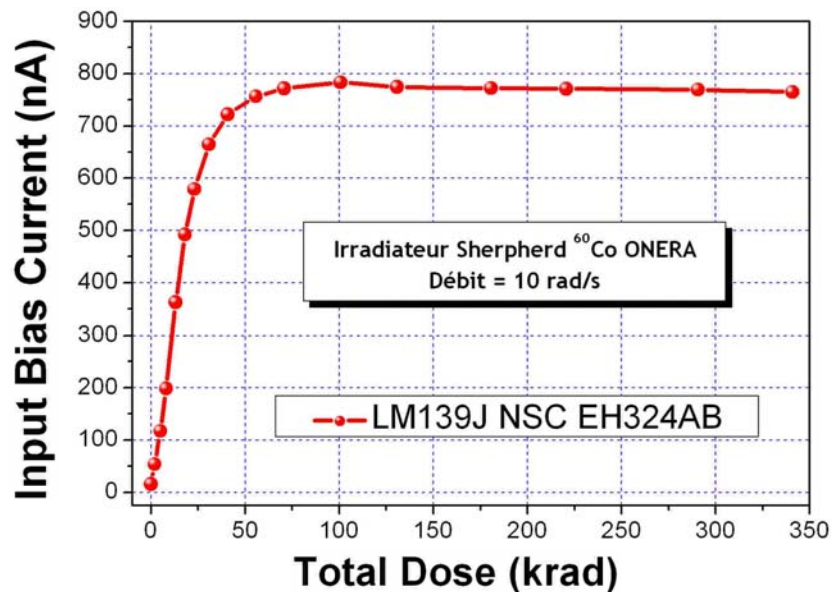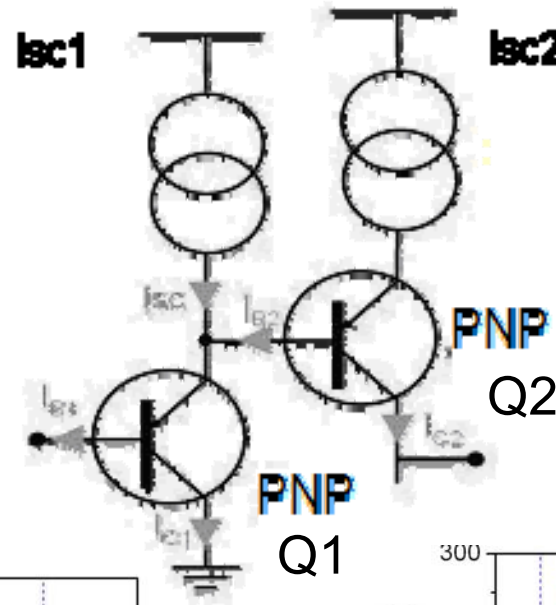


Same structure

■ LM139

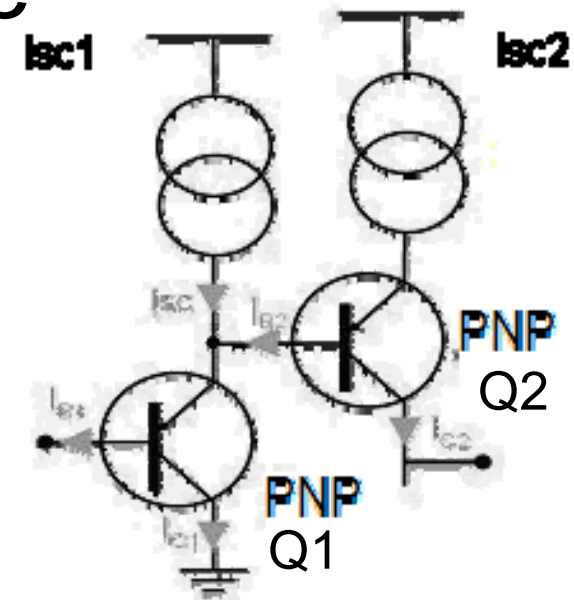- $I_{sc2} = 100\mu A$
- $I_{b2} \# \mu A \nearrow$
- $I_{sc1} \searrow \ll I_{b2}$
- $I_{e1} \approx I_{b2}$


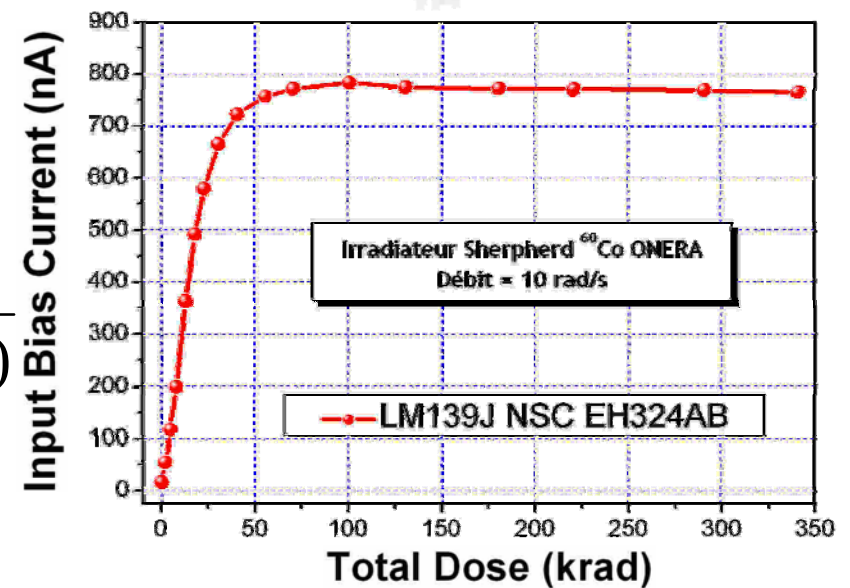
$$I_{in}(D) = \frac{I_{sc1}(D) + I_{b2}(D)}{\beta_1(D)} = \frac{I_{sc2}}{\beta_1(D) \times \beta_2(D)}$$



Same structure

■ LM124

□ $I_{sc2} = 3\mu A$

□ $I_{b2} \# nA \ll I_{sc1}$



□ $I_{e1} \approx I_{sc1}$

$$I_{in}(D) = \frac{I_{sc}(D) + \cancel{I_{b2}(D)}}{\beta_1(D)}$$

■ Two mechanisms are then to be considered



□ $\beta_1 \searrow; I_{b1} \nearrow$

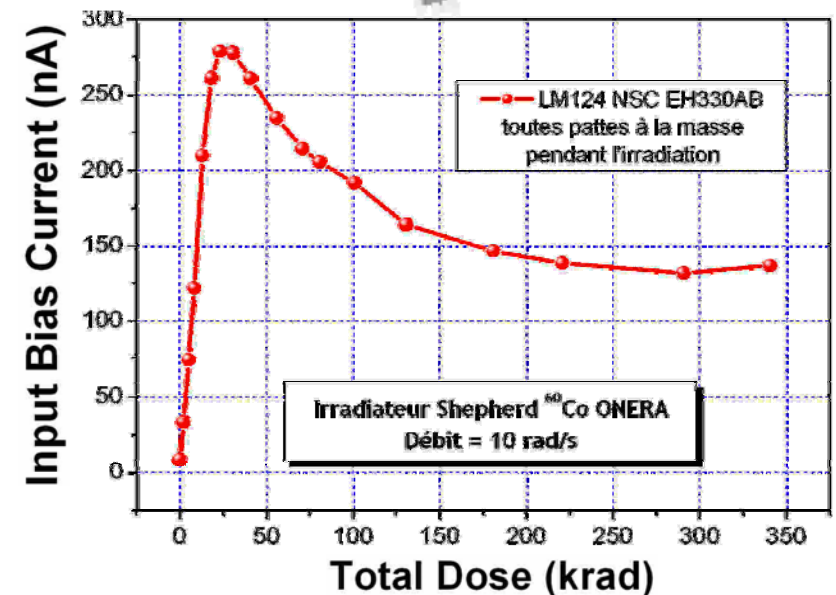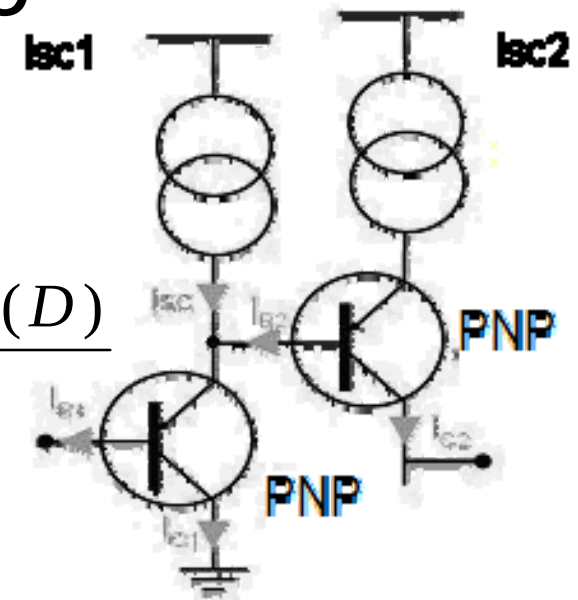□ $I_{sc1} \searrow; I_{e1} \searrow; I_{b1} \searrow$




Same structure

LM139

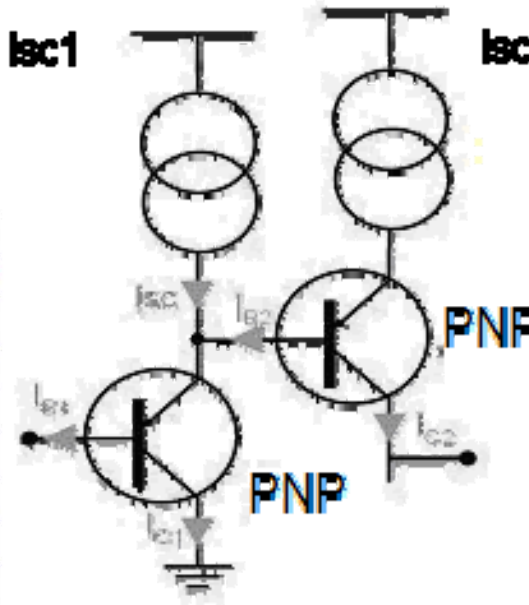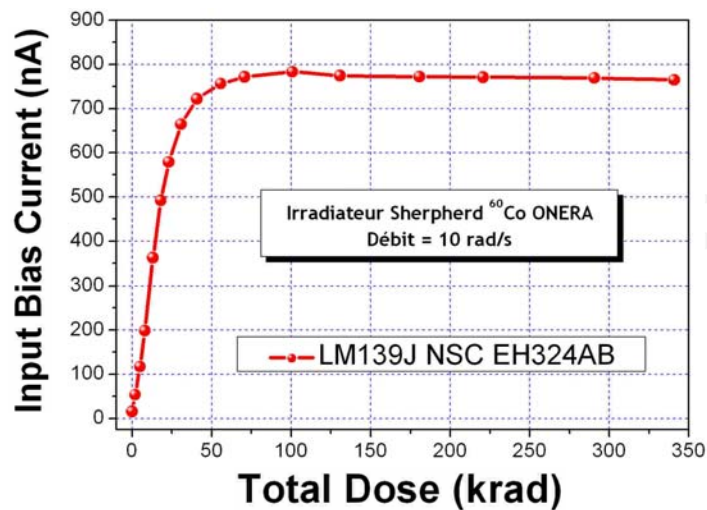

LM124

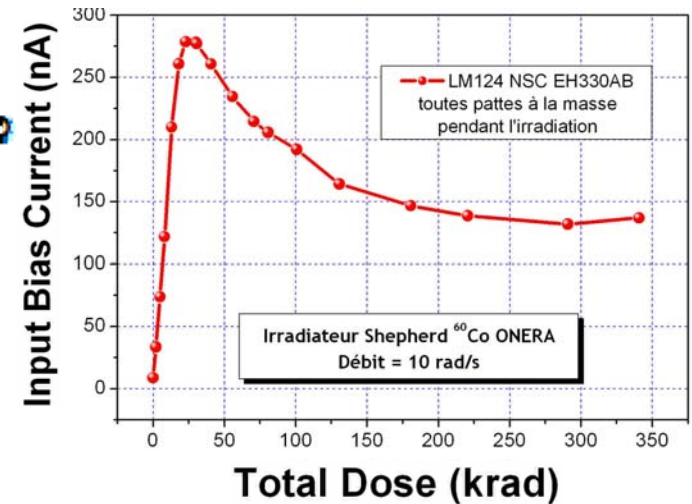


Different values of I_{sc}

Impact of bias conditions

Devices irradiated all pins grounded

- **Vbe = 0V** is a **worst case** for the degradation of **ALL** transistors
- The degradation of the current sources is maximum
- the compensation effect is maximum
- **lin+** exhibits a non monotonic shape
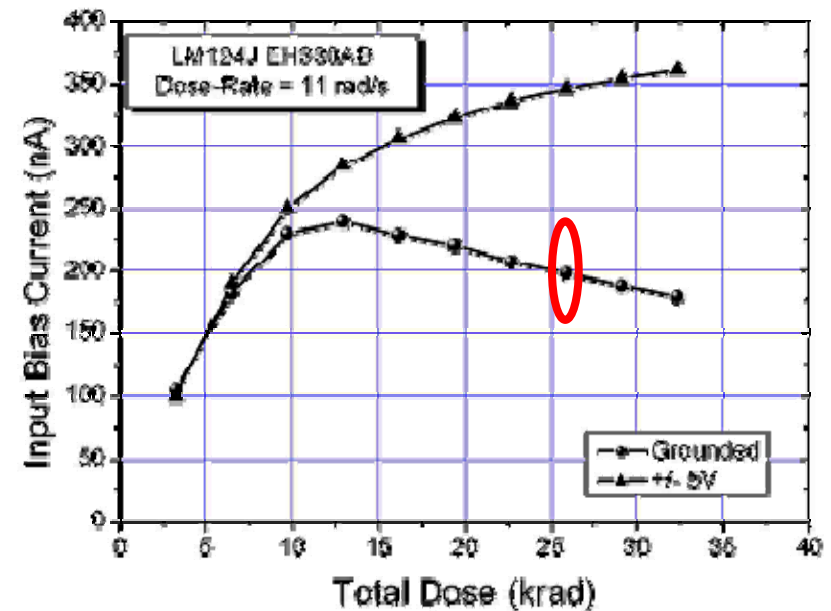
$$I_{in}(D) = \frac{I_{sc}(D)}{\beta(D)}$$




Impact of bias conditions


Devices irradiated “ON”

- The degradation of the input transistor is the same
- Current sources irradiated biased exhibit less degradation
- Compensation mechanism is reduced
- The degradation of lin^+ is Monotonic

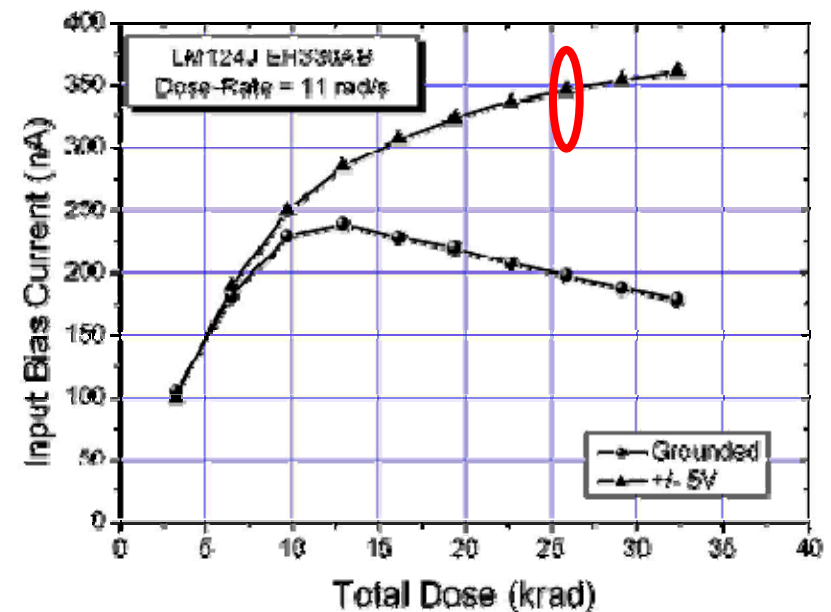
$$I_{in}(D) = \frac{I_{sc}(D)}{\beta(D)}$$



OP400 Input current canceling structures

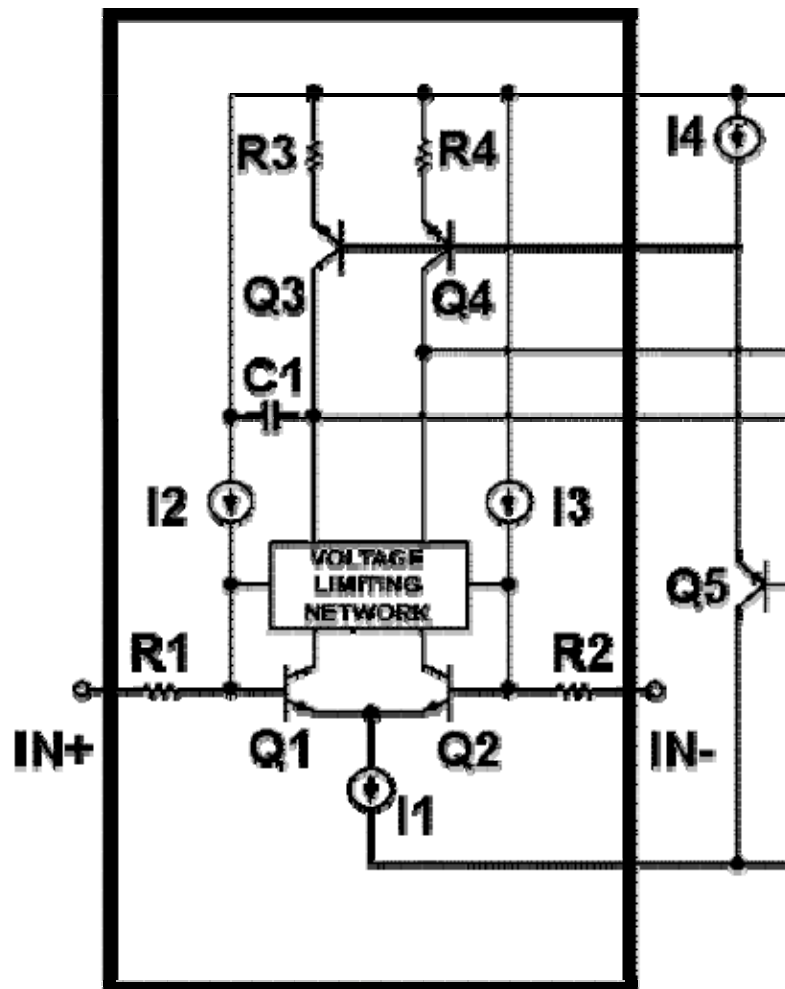


Input stage

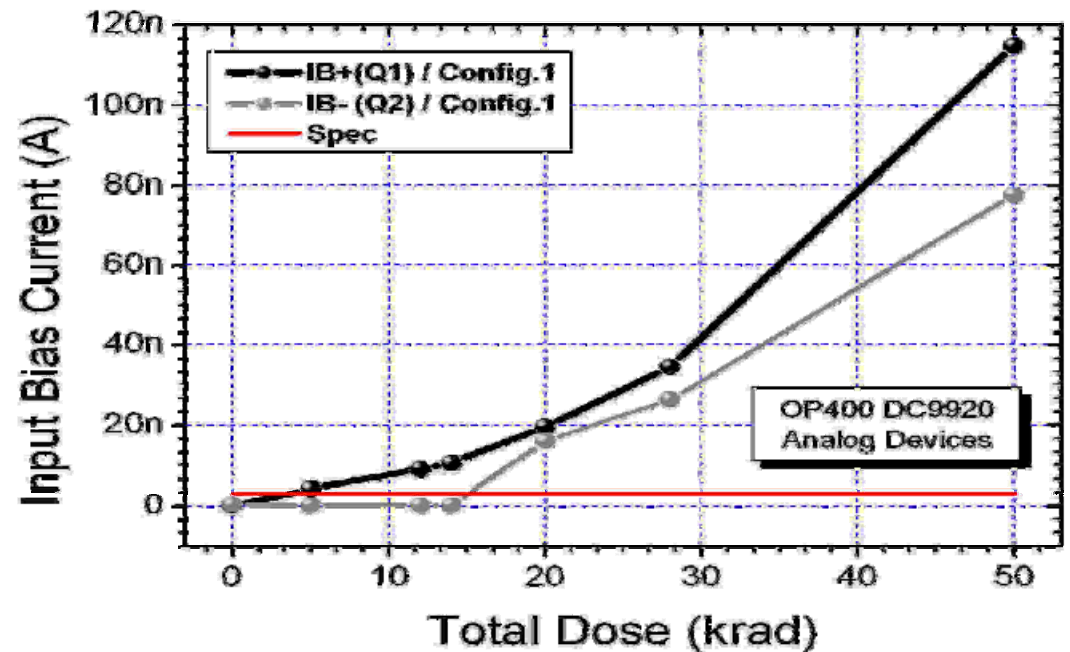

- Current Feedback cancels the bias current at the input terminals
- If current mirrors degrade, Input current increases drastically


Annealing Effect

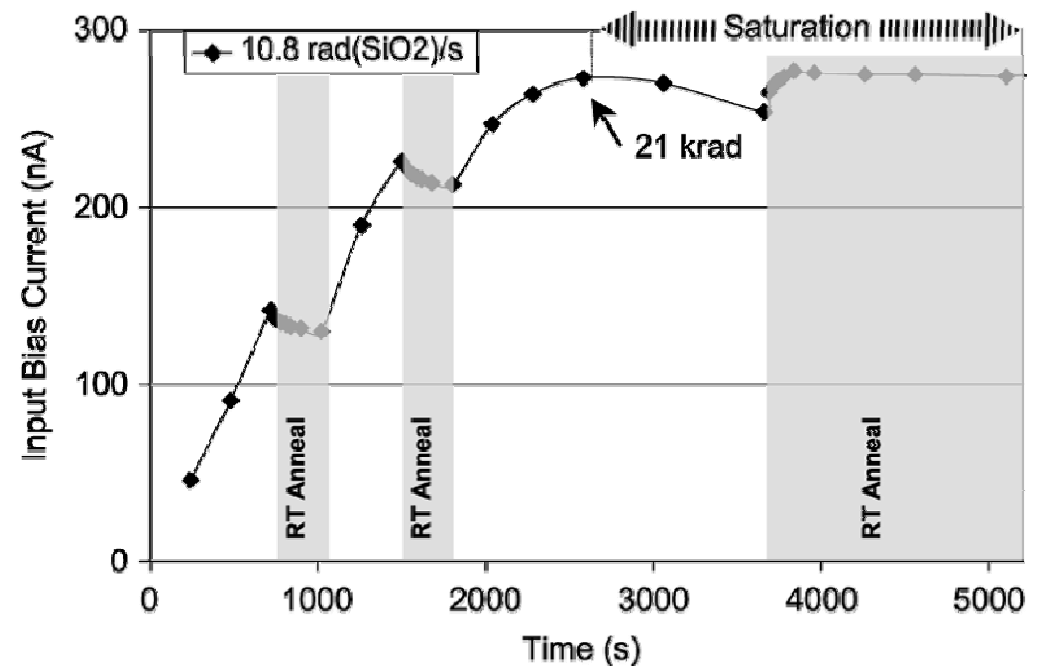- Step-stress irradiation was followed by room temperature annealing
- Annealing before saturation
 - I_{in} ↘
- Annealing after saturation
 - I_{in} ↗




Annealing Effect

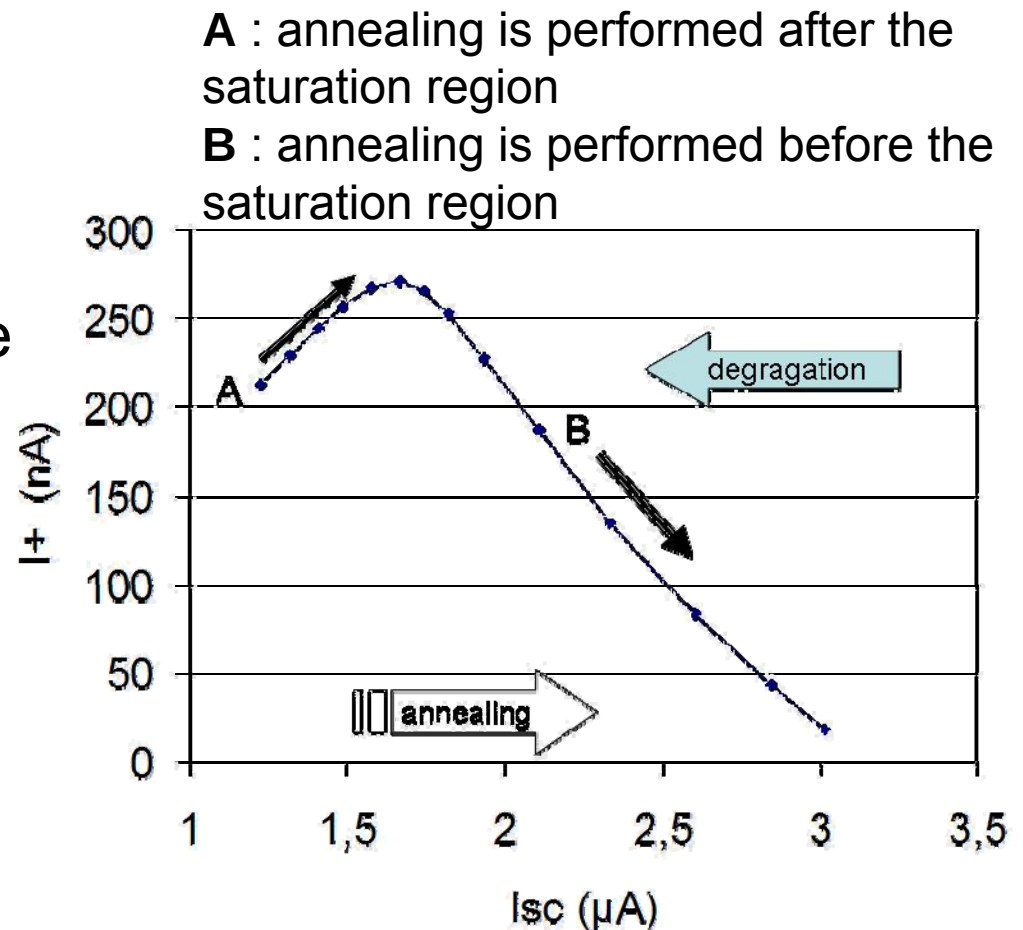- Due to compensation mechanism
 - there is a direct relationship between I_{sc} and I_{lin}
- It is possible to calculate the impact of a recovery of I_{sc} on I_{lin}
- Depending on TID, this impact can be
 - either positive (degradation)
 - negative (recovery)




➔ Annealing is not significant

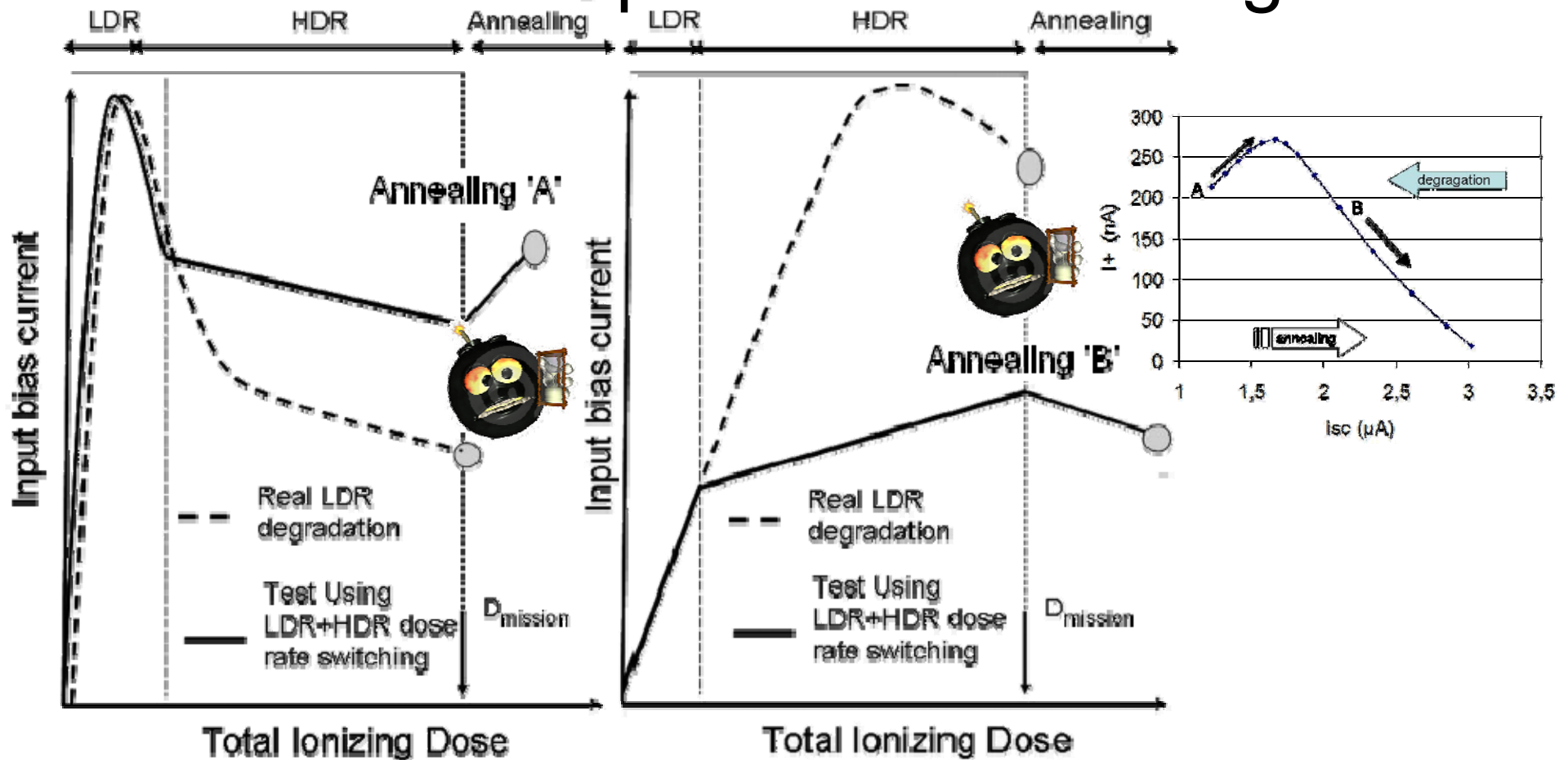Dangers of performing LDR HDR sequence + Annealing



➔ The result of LDR HDR sequence of irradiation is almost impossible to analyze

ELDRS and Dose rate switching

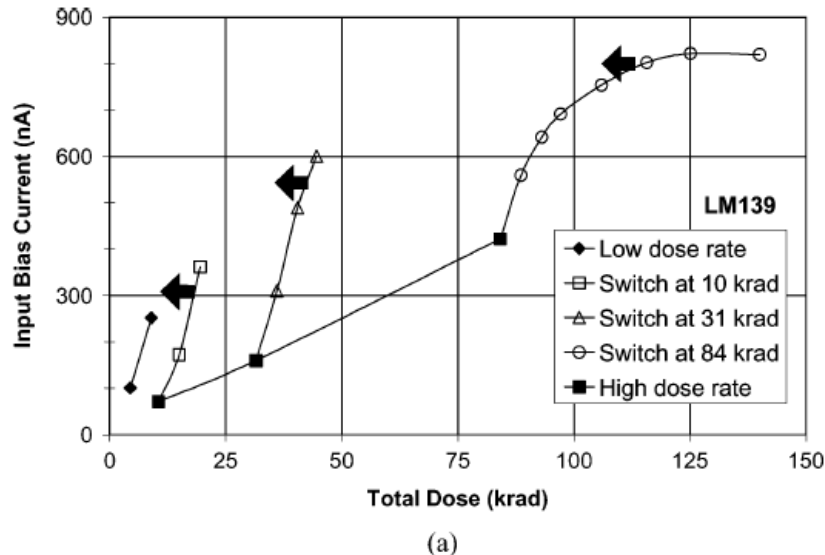


■ HDR + n LDR irradiation


□ Reconstruction of the curve by translation

□ Accurate, time saving by a factor t/n

□ requires a large sample size (n)

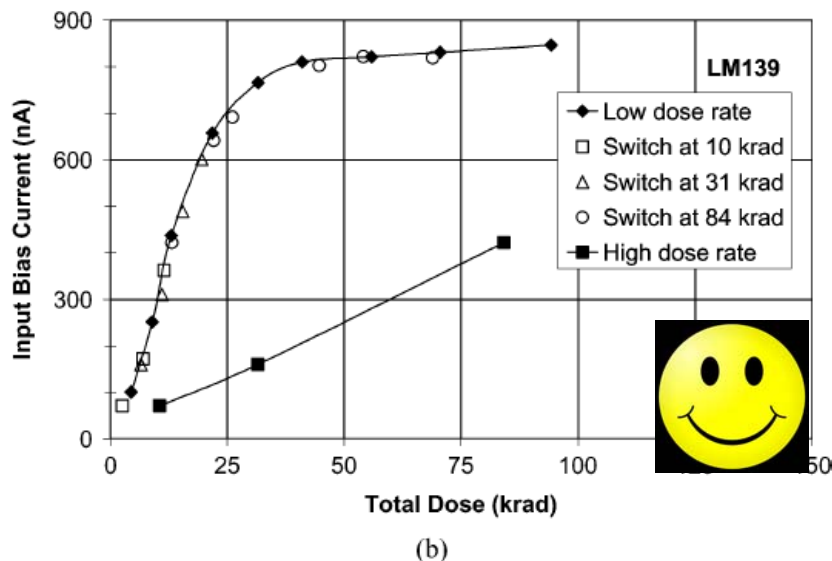

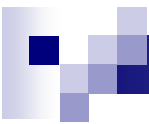J. Boch et al. "Estimation of Low Dose Rate Degradation on Bipolar Linear Integrated Circuits Using Switch-ing Experiments", IEEE Trans. Nucl. Sci., vol. 52, pp. 2616-2621, 2005



Conclusion 1/2


- The variety of shapes observed is due to circuit effects in ICs
- Compensation or cumulative degradation depends on:
 - ☐ The architecture of the input stage
 - ☐ Bias
 - ☐ Dose rate
 - ☐ Annealing

Conclusion 2/2

■ What are the risks ?

□ Missing the peak at low dose rate

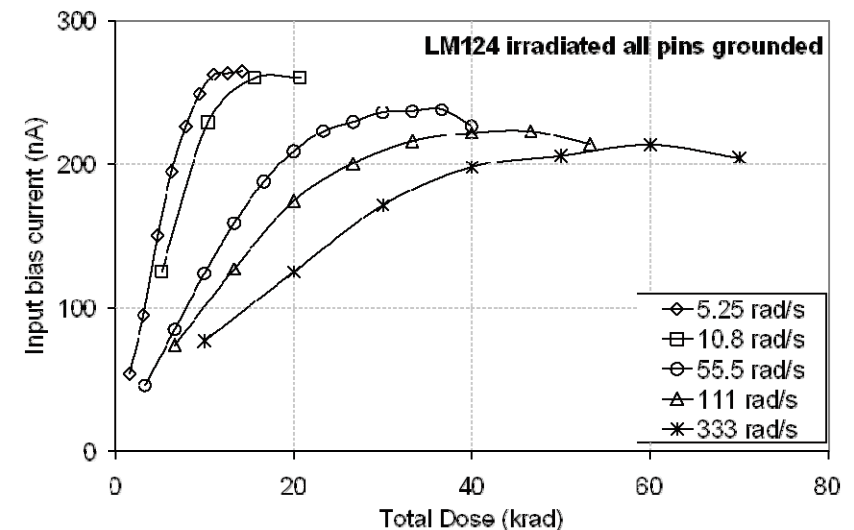- Peak value has been reported before 5krad (LDR) in some devices
- critical in the case of large irradiation steps
- Step > 15 krad





Thanks for your attention